



K-type thermocouple


Naneng 203: electric circuit

Presented to: Dr.Ahmed Sayed Abdrabou

Team: Ziad haitham, Toqa Tarek, Ali Ehab, Wafaa
Sherif

Content

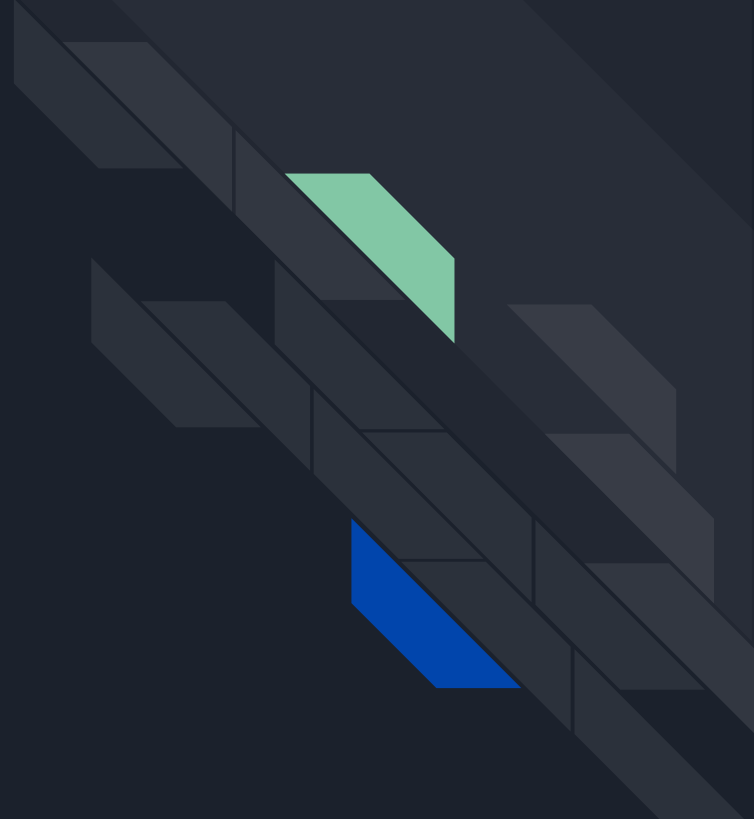1. Intro
2. Acquiring signal and displaying it
3. Signal analysis
4. Circuit design #1
5. Circuit design #2
6. Circuit design #3
7. Circuit design (hardware)
8. Spectrum of Signal







Intro


problem: measuring temperature accurately as thermocouple produce small voltage signals and may exhibit smaller voltage changes with temperature.

Solution: low-pass filter

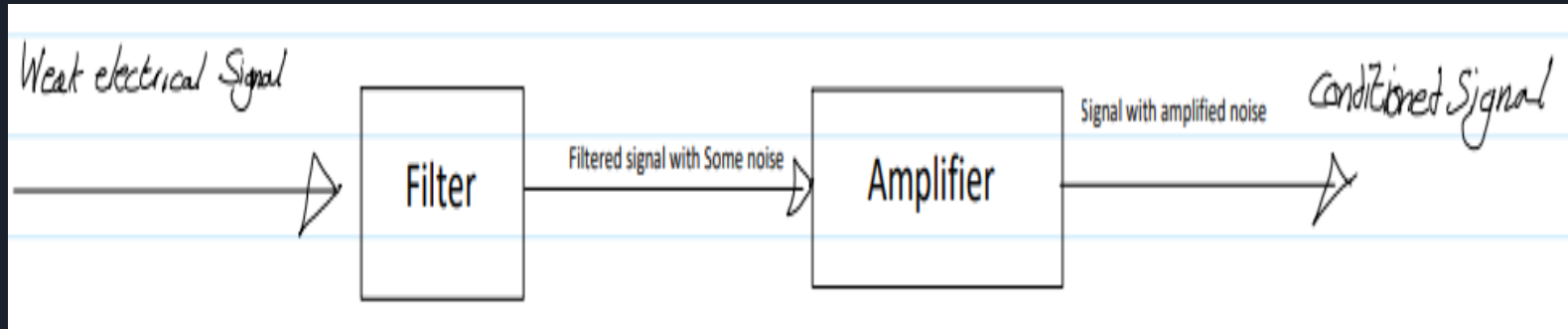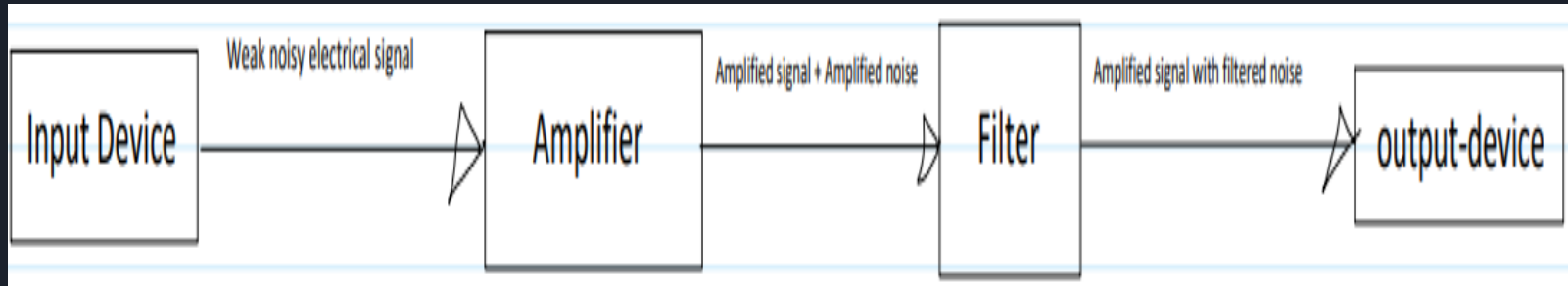


Acquiring the signal and displaying it:

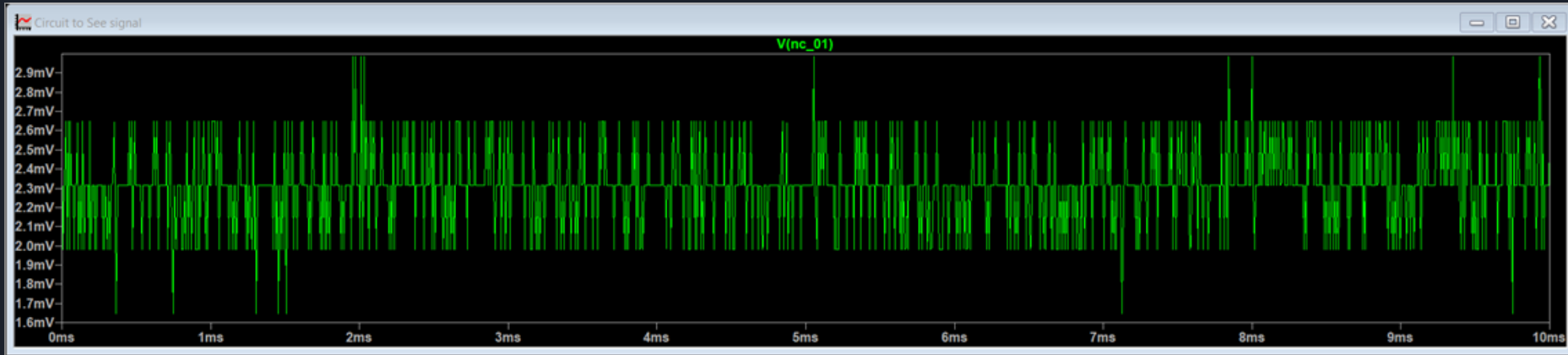- Analog discovery - Thermocouple
- Very low voltage, about 2.6 mV.





Signal Analysis:


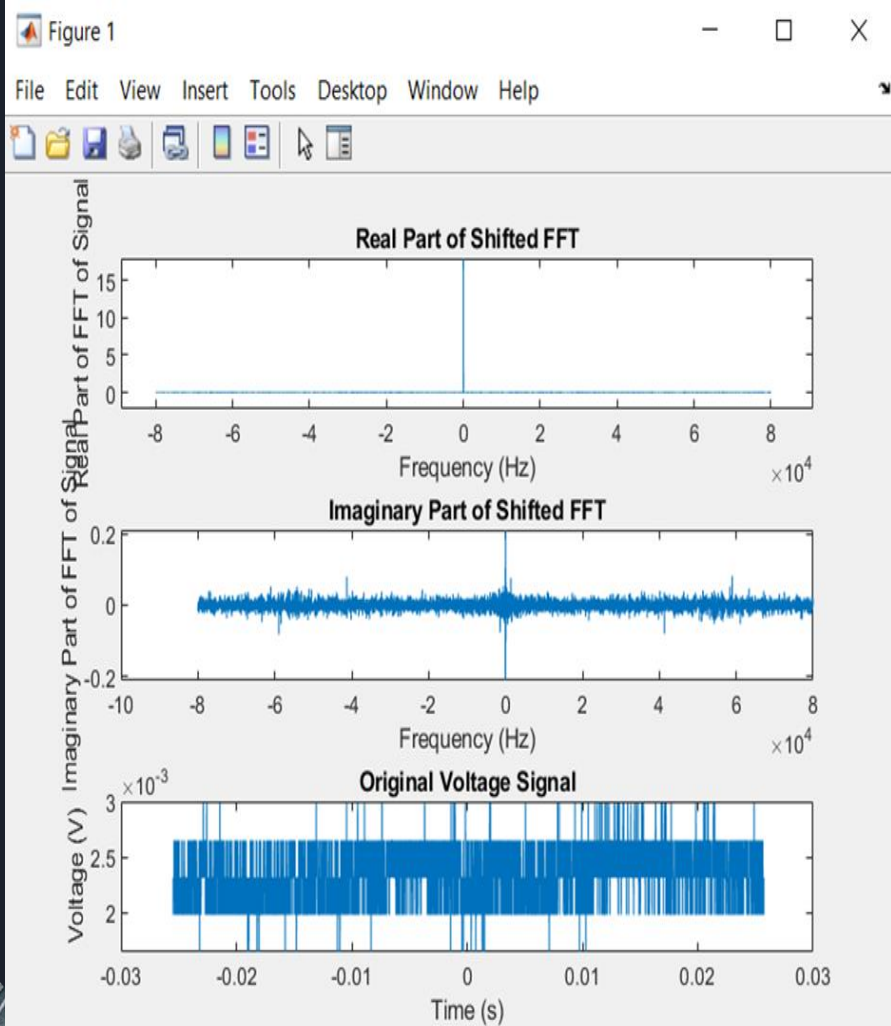
- Greatest magnitude with temperature data (desired signal)
- Rest to be filtered
- FFT(time domain \rightarrow frequency domain)





Circuit design#1:

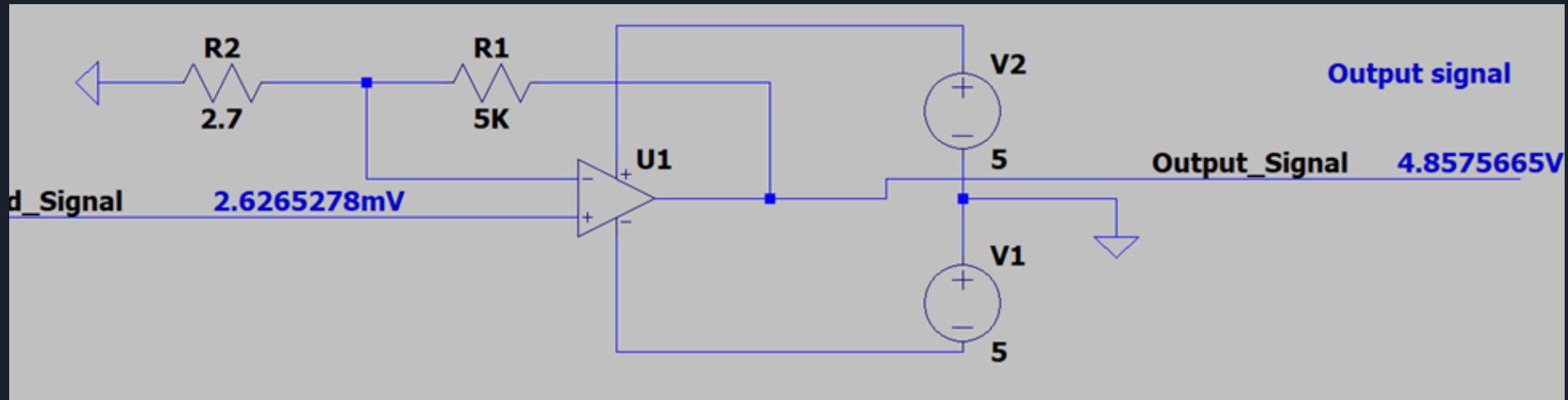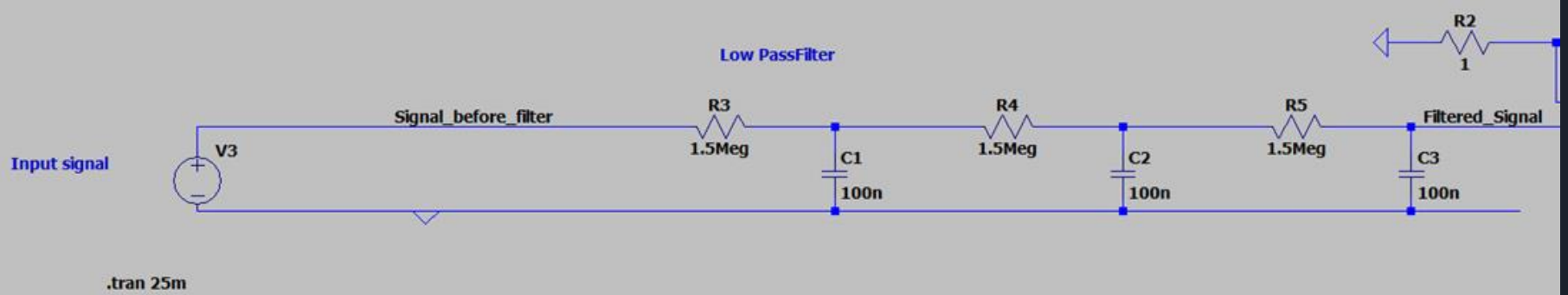


Circuit design#2:

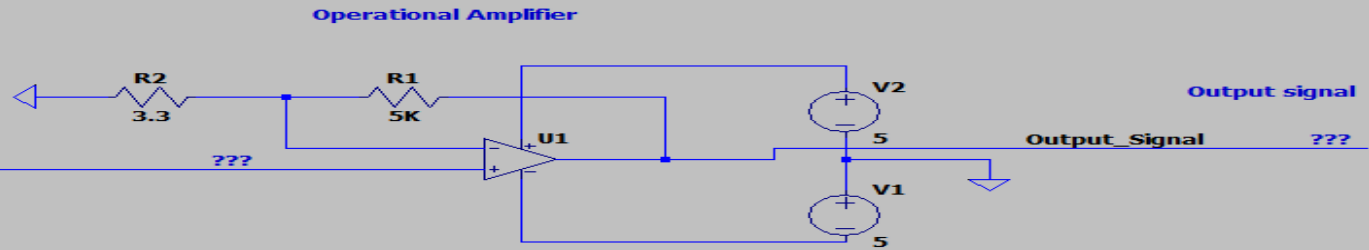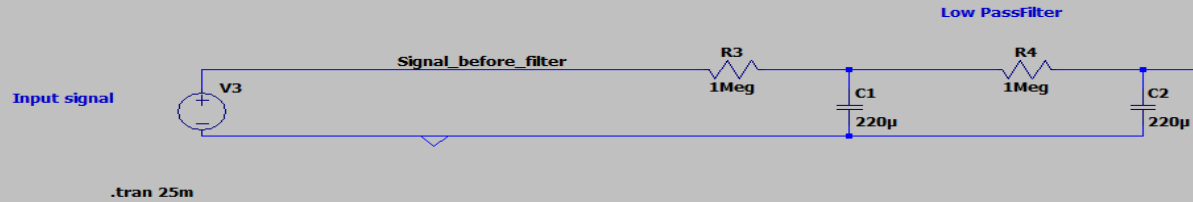


Circuit design#3:

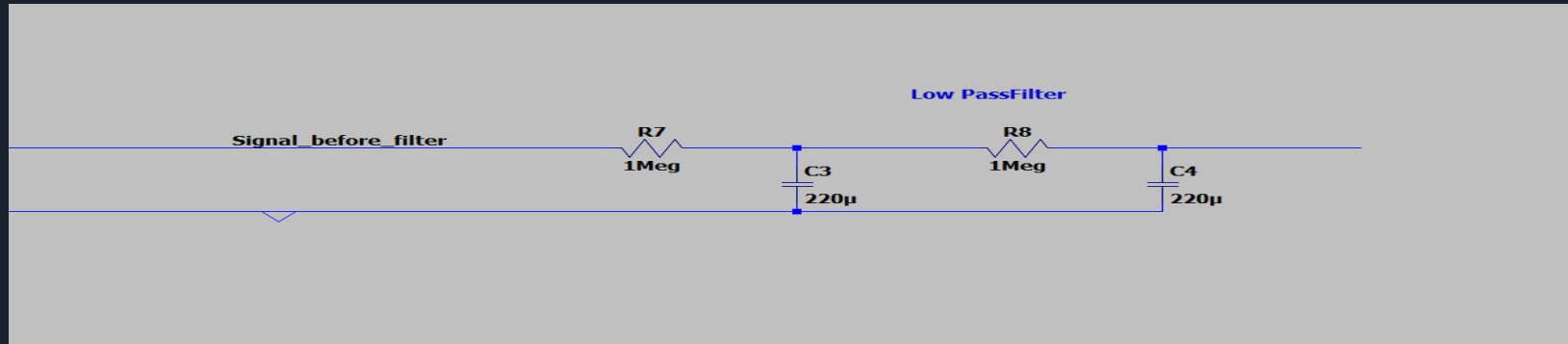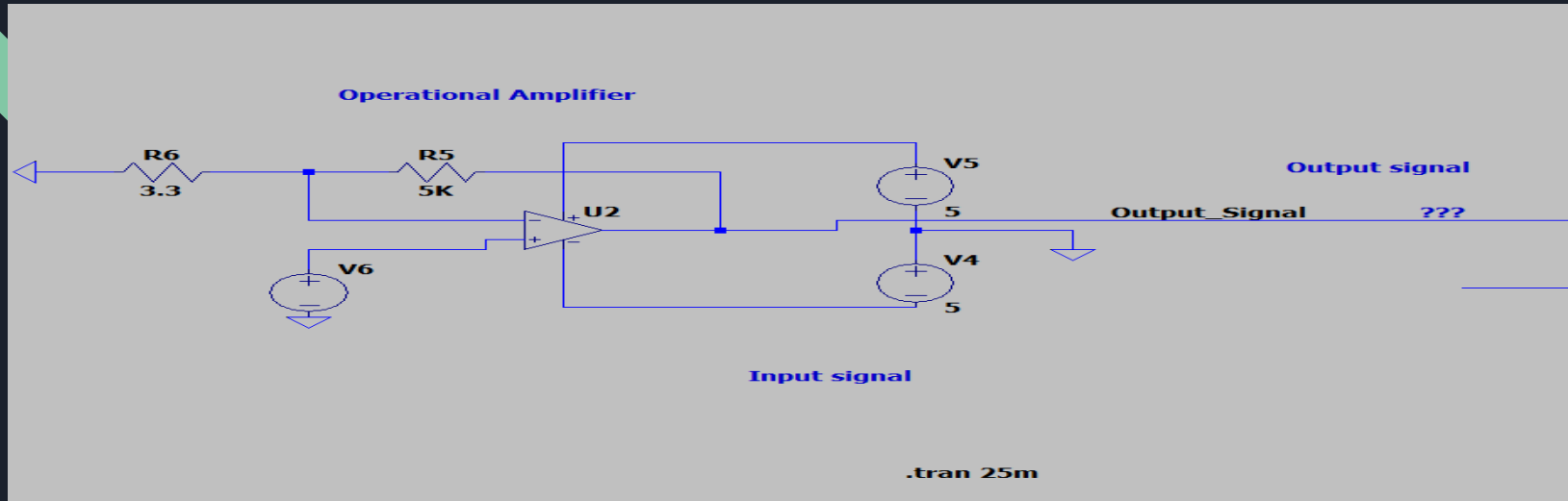


Circuit

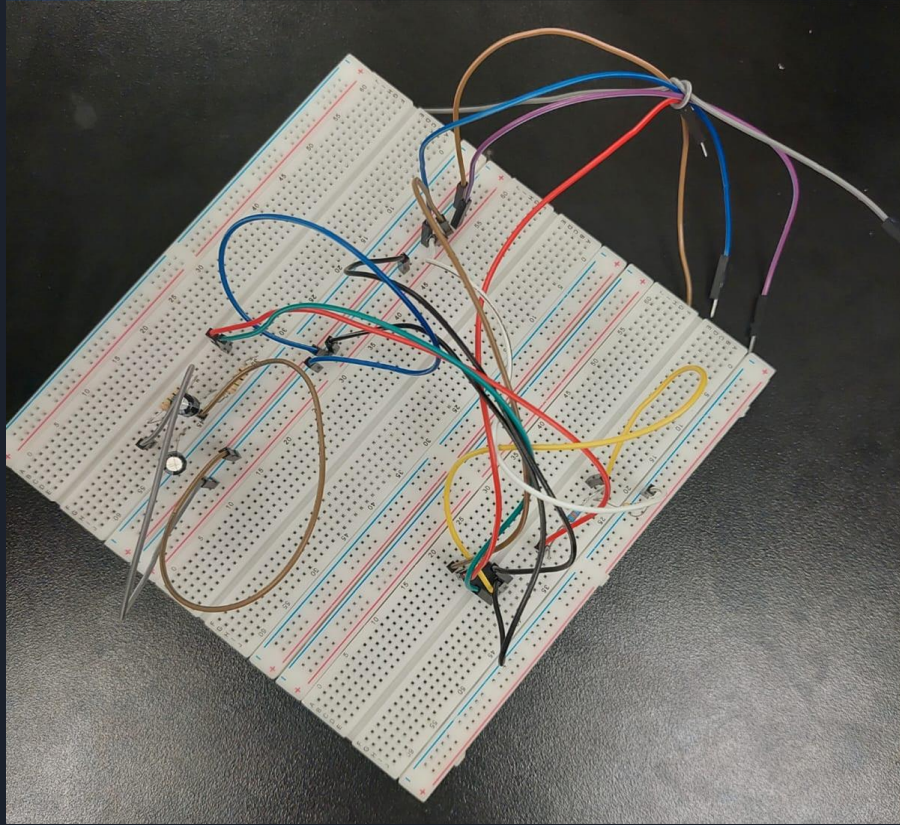

Design

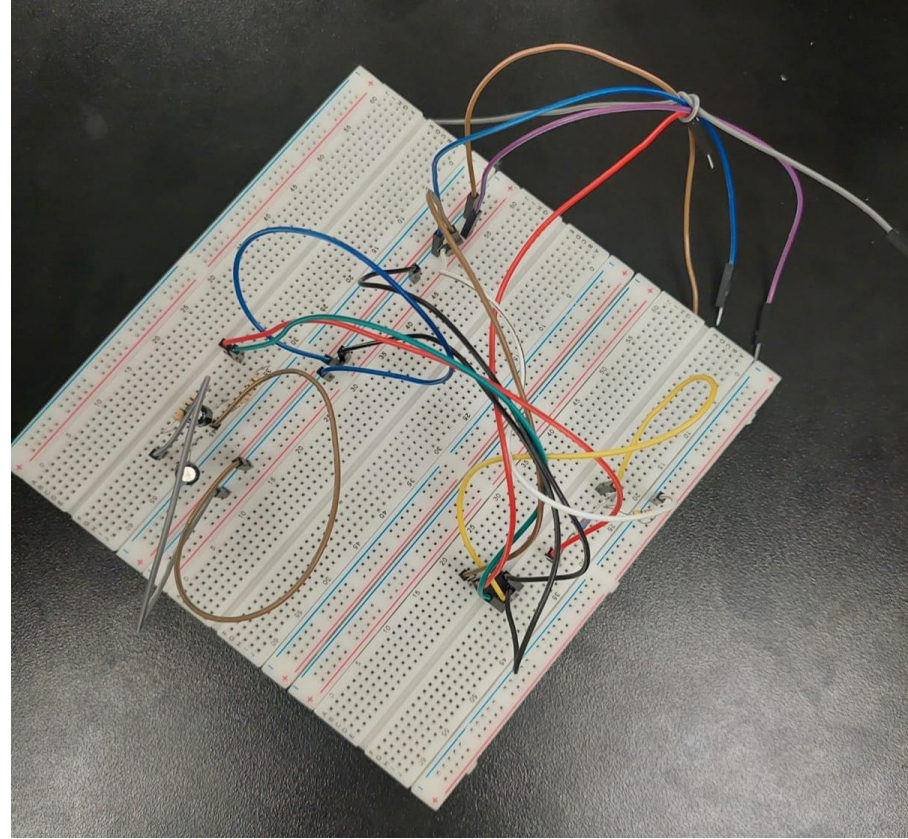


Spectrum of signal:

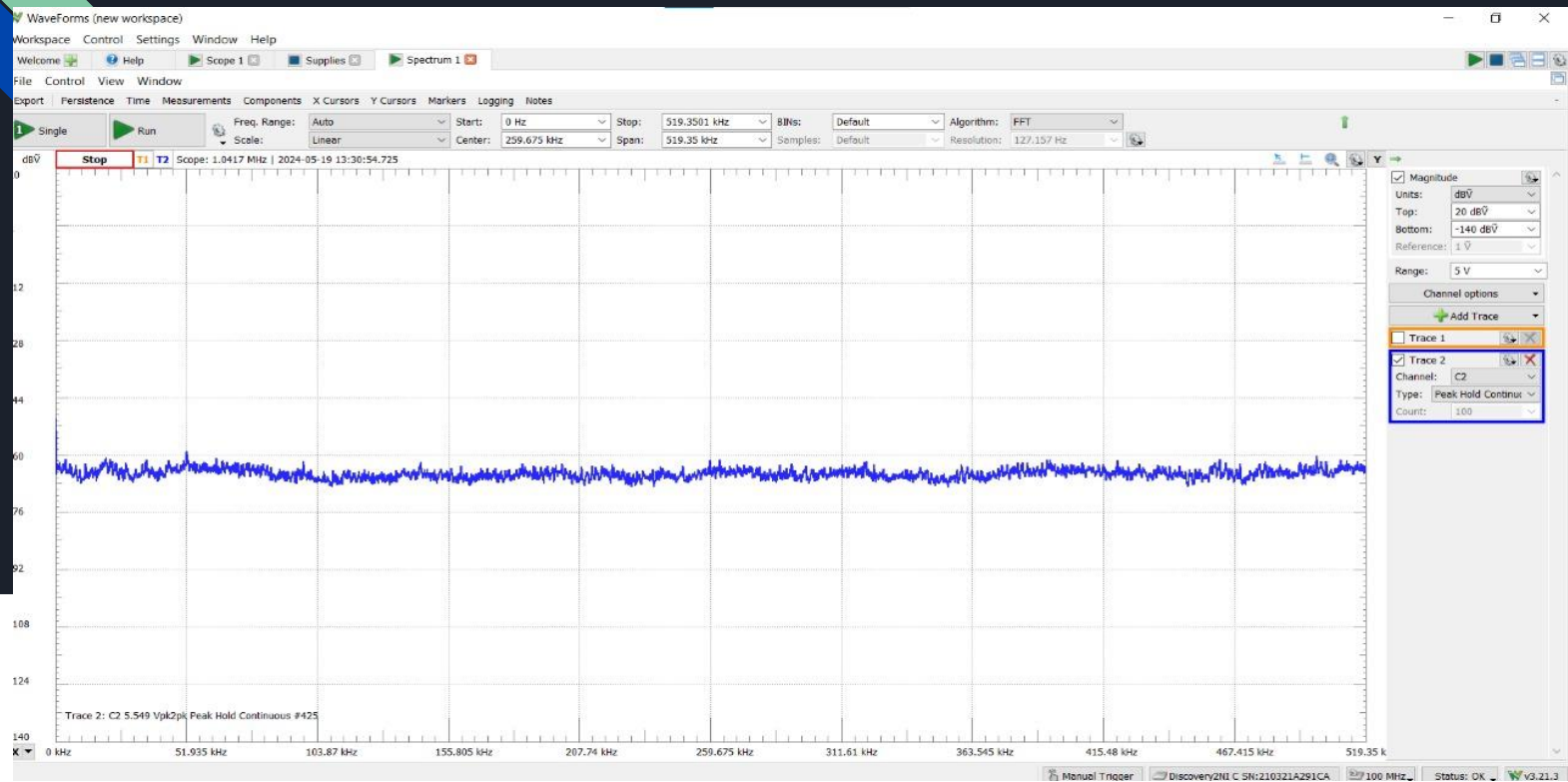

“Input signal”

Spectrum of signal:

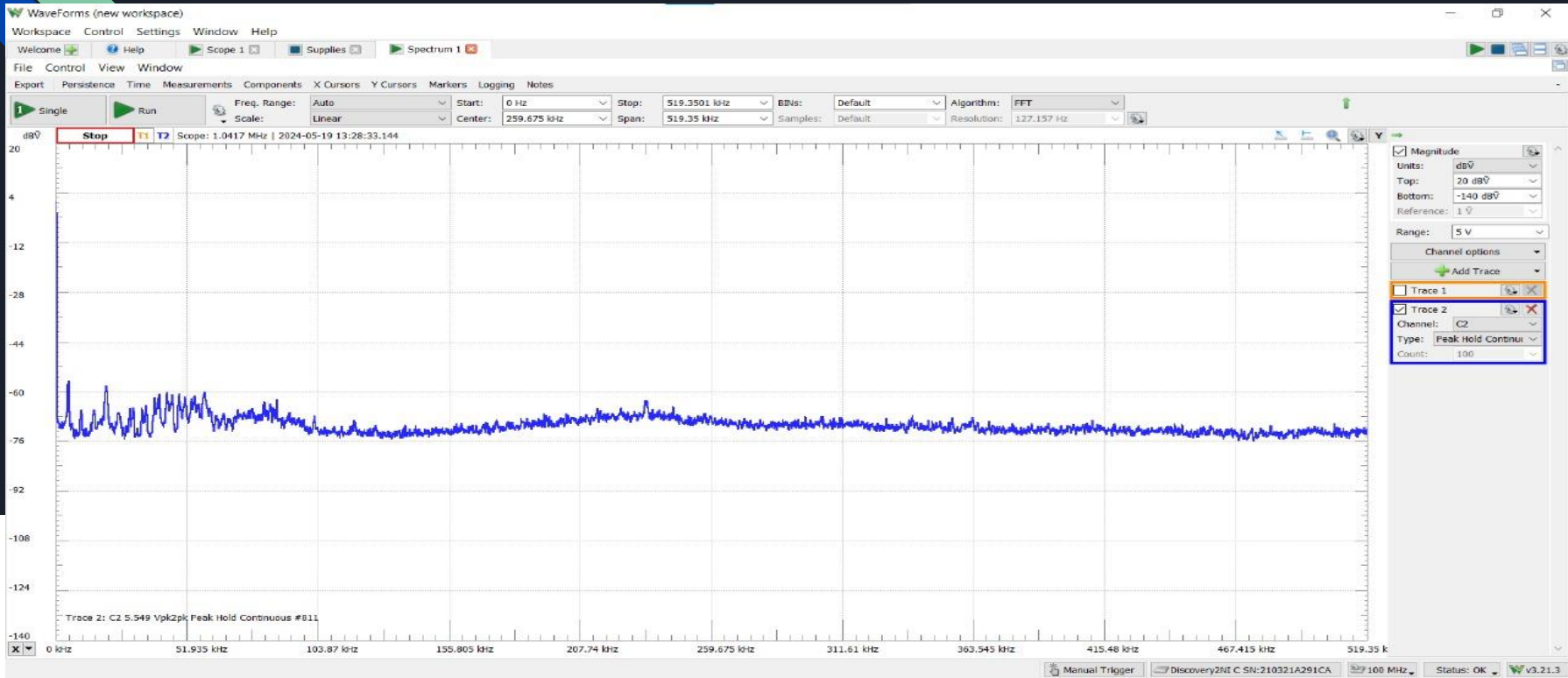

“Amplified signal”

Spectrum of signal:



“output signal(after amplification and filtration)”

Spectrum of signal:



“Input signal vs. Output signal”



Thank you